



# AN2195

## Application Note

# Tango3 and Romeo2 Layout Recommendations

## Introduction

Tango3 (MC33493) is a UHF transmitter IC and Romeo2 (MC33591/2/3) is a UHF receiver IC. They are designed for remote keyless and remote control applications along with any other ISM applications. Special care concerning the PCB layout must be considered to prevent application issues. A poor layout may result in degraded performances (high transmission spurious with Tango3 or low sensitivity with Romeo2) or even worse, in non-functionalities.

This application note provides some recommendations for the proper use of Romeo2 and Tango3.

## Tango3 Layout Recommendations

### Crystal placement

The crystal unit must be placed as close as possible to the  $X_{TAL1}$  and  $X_{TAL0}$  pins; the  $X_{TAL1}$  track also needs to be minimized. It should, ideally, be shielded by a ground plan around the crystal unit and a ground plane below the crystal unit (on the opposite side of the board).

The purpose of this shielding is to minimize parasitic-coupled harmonics of the crystal frequency in the transmitted power and also to prevent the crystal oscillator from being disturbed by external EMC noise or parasitic couplings. The shielding plan will have a capacitor effect which must be taken into account in order to calculate the right load capacitor for the expected carrier frequency and deviation in FSK modulation.

When the crystal cannot be shielded, the designer must take care if a digital track is running in the crystal oscillator neighborhood or beneath the crystal unit, that no voltage is toggled while the Tango3 oscillator is enabled (Enable pin = High). Otherwise, it may introduce phase transient shifts in FSK modulation or even a transient oscillator stop.

## Romeo2 Layout Recommendations

### CFSK

The CFSK track length must be minimized in a FSK application. The longer the track length, the more parasitic capacitance produced and the more it will affect the frequency deviation. Therefore, it must be minimized so that the frequency deviation is compliant with the expected deviation.

### Decoupling capacitances

The decoupling capacitances must be very close to the  $V_{CC}$  and GND pins. If the track lengths between the capacitances and the product pins are too long, the  $V_{CC}$  pins cannot be considered as a ground for RF frequencies. It could impact the matching of the Tango3 RF output with the antenna and subsequently the radiated output power.

The recommended decoupling capacitances are 100 pF and 10 nF.

### Dataclock

The dataclock driver requires a very small capacitive load. If the length of the dataclock track is too long or if additional capacitances (like a standard oscilloscope probe) are added onto this track, the dataclock signal may become a trapezoidal or triangular shaped signal. For this reason, the track must be shortened as much as possible.

## Romeo2 Layout Recommendations

### Crystal placement

The crystal must be placed as close as possible to the  $X_{TAL1}$  and  $X_{TAL2}$  pins; also, the  $X_{TAL1}$  track length must be minimized. Ideally, it should be shielded by a ground plan around the crystal unit and a ground plane below the crystal unit (on the opposite side of the board).

The purpose of this shielding is to prevent the crystal oscillator from being disturbed by external EMC noise or parasitic couplings. The shielding plan will have a capacitive effect which must be taken into account in order to design the right load capacitor for the expected local oscillator frequency.

When the crystal cannot be shielded, the designer must take care, if a digital track is running in the crystal neighborhood or beneath the crystal, that no output port is toggled while the Romeo2 oscillator is enabled. Otherwise, it may introduce transient phase shifts of local oscillator which may result in data loss in FSK).

### PFD


The PFD pin can, theoretically, be non-connected. But, since the PFD voltage controls the  $V_{CO}$ , it is a “sensitive input” and any coupled noise or signal will result in phase noise of the local oscillator or will shift its frequency. Thus, it is ideal to implement the external filter that is proposed in the MC33591 data sheet.

## Decoupling capacitances

The decoupling capacitances must be very close to the  $V_{CC}$  and  $V_{CC}LNA$  (pins 1, 2, and 3) and to the  $GNDLNA$  and  $GNDSUB$  pins. In addition, special care must be considered for the ground plane connecting the  $GNDV_{CO}$ ,  $GNDSUB$ , and  $GNDLNA$  pins.

## RFin

$RF_{in}$  is a biased input. Therefore, to avoid any DC conflict between Romeo2 and an external device, it is recommended that a DC decoupling capacitance be inserted. The DC decoupling capacitance acts as a short circuit at the RF frequencies (for example, a 100 pF to 1 nF capacitance.)

Motorola reserves the right to make changes without further notice to any products herein. Motorola makes no warranty, representation or guarantee regarding the suitability of its products for any particular purpose, nor does Motorola assume any liability arising out of the application or use of any product or circuit, and specifically disclaims any and all liability, including without limitation consequential or incidental damages. "Typical" parameters can and do vary in different applications and actual performance may vary over time. All operating parameters, including "Typicals", must be validated for each customer application by customer's technical experts. Motorola does not convey any license under its patent rights nor the rights of others. Motorola products are not designed, intended, or authorized for use as components in systems intended for surgical implant into the body, or other applications intended to support or sustain life, or for any other application in which the failure of the Motorola product could create a situation where personal injury or death may occur. Should Buyer purchase or use Motorola products for any such unintended or unauthorized application, Buyer shall indemnify and hold Motorola and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs, damages, and expenses, and reasonable attorney fees arising out of, directly or indirectly, any claim of personal injury or death associated with such unintended or unauthorized use, even if such claim alleges that Motorola was negligent regarding the design or manufacture of the part. Motorola and  are registered trademarks of Motorola, Inc. Motorola, Inc. is an Equal Opportunity/Affirmative Action Employer.

MOTOROLA and the Stylized M Logo are registered in the US Patent & Trademark Office. All other product or service names are the property of their respective owners. © Motorola, Inc. 2001.

#### HOW TO REACH US:

**USA/EUROPE/LOCATIONS NOT LISTED:** Motorola Literature Distribution: P.O. Box 5405, Denver, Colorado 80217.  
1-303-675-2140 or 1-800-441-2447

**JAPAN:** Motorola Japan Ltd.; SPS, Technical Information Center, 3-20-1 Minami-Azabu. Minato-ku, Tokyo 106-8573 Japan.  
81-3-3440-3569

**ASIA/PACIFIC:** Motorola Semiconductors H.K. Ltd.; Silicon Harbour Centre, 2 Dai King Street, Tai Po Industrial Estate, Tao Po, N.T., Hong Kong. 852-26668334

**TECHNICAL INFORMATION CENTER: 1-800-521-6274**

**HOME PAGE:** <http://motorola.com/semiconductors/>



**MOTOROLA**

AN2195/D

**SUNSTAR 商斯达实业集团**是集研发、生产、工程、销售、代理经销、技术咨询、信息服务等为一体的高科技企业，是专业高科技电子产品生产厂家，是具有 10 多年历史的专业电子元器件供应商，是中国最早和最大的仓储式连锁规模经营大型综合电子零部件代理分销商之一，是一家专业代理和分销世界各大品牌 IC 芯片和电子元器件的连锁经营综合性国际公司，专业经营进口、国产名厂名牌电子元件，型号、种类齐全。在香港、北京、深圳、上海、西安、成都等全国主要电子市场设有直属分公司和产品展示展销窗口门市部专卖店及代理分销商，已在全国范围内建成强大统一的供货和代理分销网络。我们专业代理经销、开发生产电子元器件、集成电路、传感器、微波光电元器件、工控机/DOC/DOM 电子盘、专用电路、单片机开发、MCU/DSP/ARM/FPGA 软件硬件、二极管、三极管、模块等，是您可靠的一站式现货配套供应商、方案提供商、部件功能模块开发配套商。商斯达实业公司拥有庞大的资料库，有数位毕业于著名高校——有中国电子工业摇篮之称的西安电子科技大学（西军电）并长期从事国防尖端科技研究的高级工程师为您精挑细选、量身订做各种高科技电子元器件，并解决各种技术问题。

更多产品请看本公司产品专用销售网站：

商斯达中国传感器科技信息网：<http://www.sensor-ic.com/>

商斯达工控安防网：<http://www.pc-ps.net/>

商斯达电子元器件网：<http://www.sunstare.com/>

商斯达微波光电产品网：[HTTP://www.rfoe.net/](http://www.rfoe.net/)

商斯达消费电子产品网：<http://www.icasic.com/>

商斯达实业科技产品网：<http://www.sunstars.cn/>

传感器销售热线：

地址：深圳市福田区福华路福庆街鸿图大厦 1602 室

电话：0755-83370250 83376489 83376549 83607652 83370251 82500323

传真：0755-83376182 (0) 13902971329 MSN: [SUNS8888@hotmail.com](mailto:SUNS8888@hotmail.com)

邮编：518033 E-mail:[szss20@163.com](mailto:szss20@163.com) QQ: 195847376

深圳赛格展销部：深圳华强北路赛格电子市场 2583 号 电话：0755-83665529 25059422

技术支持：0755-83394033 13501568376

欢迎索取免费详细资料、设计指南和光盘；产品凡多，未能尽录，欢迎来电查询。

北京分公司：北京海淀区知春路 132 号中发电子大厦 3097 号

TEL: 010-81159046 82615020 13501189838 FAX: 010-62543996

上海分公司：上海市北京东路 668 号上海赛格电子市场 2B35 号

TEL: 021-28311762 56703037 13701955389 FAX: 021-56703037

西安分公司：西安高新开发区 20 所(中国电子科技集团导航技术研究所)

西安劳动南路 88 号电子商城二楼 D23 号

TEL: 029-81022619 13072977981 FAX:029-88789382